

ASSIGNMENT- Science

CHAPTER 11

Q1. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?

Q2. In Parallel circuits if 10 resistors each of them are ohm are connected parallel, and then what will be total resistant?

Email: techtutor.megh@gmail.com