

Assignment

Chapter 11 | 11.6.1 Resistors in Series

Question

1. Draw a schematic diagram of a circuit consisting of a battery of three cells of 2V each, a 5Ω resistor, an 8Ω resistor and a 12Ω resistor, and a plug key, all connected in series.

Email to: techtutor.megh@gmail.com