

Assignment

Chapter 11 | 11.6.2 Resistors in Parallel

Question

1. What are the advantages of connecting electrical devices in parallel with the battery instead of connecting them in series?
2. Why is the series arrangement not used for domestic circuits?

Email to: techtutor.megh@gmail.com